

# The Phasing Transceiver on 73kHz

Part one of a two part article by John R Hey, G3TDZ\*



**T**HE PHASING TRANSCEIVER which was described in *RadCom* in July and August 1993 still forms the core of my main amateur station. As this has been a success, when the new 73kHz band came along, there seemed little point in developing a new circuit, especially as the printed boards are still available off the shelf.

At such a low frequency, there seems little point in superhet technique; direct conversion on both receive and transmit would seem the obvious path to explore. Here a small admission seems proper: almost two years ago, a pair of LF SSB radios were built for caving use and have proved themselves. With all the experimentation already done, it was only necessary to build another, this time with a VFO replacing the crystal and the S meter and CW filter reintroduced.

## THE RECEIVER

THE CASCODE RF amp and VFO amplifier components are omitted from the receiver board. In their place, a small piggy-back board houses the RF amp which now employs a very low noise HF op-amp OP-37. A single input tuned circuit may be used with any antenna input but when connected via the relay, forms with a series tuned loop antenna, a bottom capacity coupled pair with a working Q of 14.

The quadrature pair of injections to the two

mixers comes from a divider on the exciter board. **Fig 1** shows the mounting method and **Fig 2** the modified circuitry.


Readers who missed the original articles and would like a copy of the complete receiver may contact me at the address given on this page.

## THE TRANSMITTER

BECAUSE THERE ARE many more changes, the transmitter is drawn in its entirety and will be shown in the diagram next month. It is very much easier to build a stable VFO at about 4.5MHz and divide down than to try and wind a 390µH coil for 73kHz.

The VFO is already very stable; when divided by 64 it is remarkably so. Where desired, crystal control is easy. These components are omitted where the VFO feeds pin 11 of the 4060 divider. The following 4013 divides a further four times and generates the I and Q quadrature signals for both transmitter and receiver. At this low frequency, a DPDT front panel switch enables easy sideband selection.

IC1 performs mic amplifier, low-pass filter, drive for the phase shift networks, and centre rail

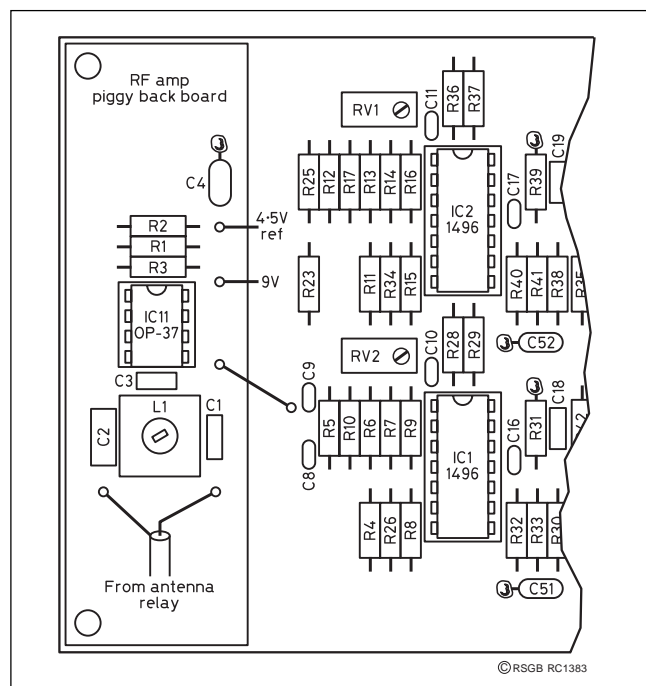

**Fig 1:** Modified receiver component layout showing the new piggy-back board with the 73kHz components.

\*8 Armley Grange Crescent, Leeds LS12 3QL.


reference voltage generator. The phasing networks are buffered by IC2 where audio level equalising is made possible by R25 and RV1. Points A and B should be connected to A and B on the balanced modulators IC3 and IC4 by wires under the board.

The trimpot RV3 equalises conversion gain and RV2 and RV4 are carrier balance. The two modulators are terminated in the tuned circuit L1, C26 which are mounted on the power amp board. Here a car radio audio power chip TDA2003 completes the circuit.

But where is the output tuned circuit and low-pass filter you are asking. As the output resistance is less than an ohm, these would be hard to design - but more on this next month.
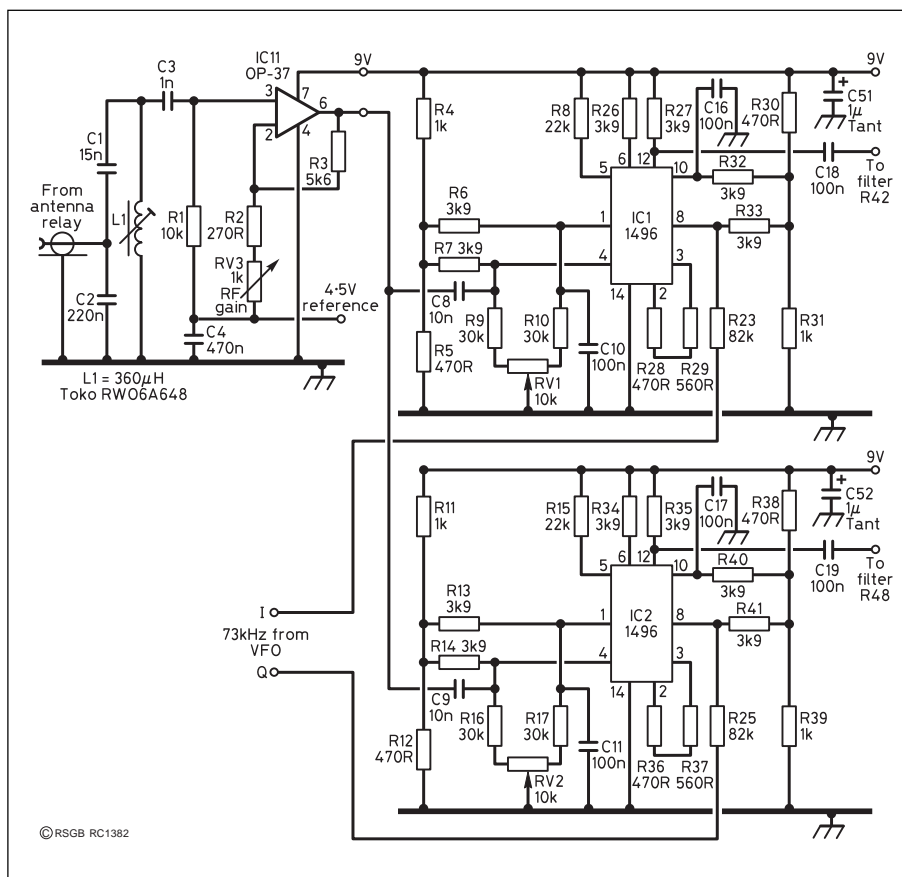
## THE ANTENNA

IN THE SEPTEMBER 1996 *RadCom* 73LF page, a loop antenna was described. A multi-turn loop will not transmit an E wave but makes an excellent receiving antenna. Unwanted beacons can be nulled out by careful rotation. If a tap four turns up from the earthy end is provided, a long wire such as a topband antenna can be connected and will radiate. A long wire on a kite or balloon, or a barbed wire fence, should radiate better. ♦



... to be continued

Fig 2: Modified circuitry of the 73kHz section of the receiver.

## SOFTWARE FOR THE RADIO AMATEUR

Europe's leading distributor of Amateur Radio, Engineering and Communications Shareware/PD programs for the PC. 100's of related program disks - FREE CATALOGUE

## Transmit and Receive

### SSTV - FAX - RTTY - CW - AMTOR

This BRITISH made interface for the PC is built into a 25 way EMC/RFI proof 'D' Connector. Comes complete with interface cable & 3 software packages.

As featured in HRT, PW, SWM, DATACOM, Break-in New Zealand & CQ Ham Radio Japan. Only £49.95 plus postage.

<http://www.venuswww.demon.co.uk>

## VENUS ELECTRONICS

26 Pevensey Way, Frimley Green, Camberley, Surrey GU16 5YJ Tel/Fax: 01252 837860 E-mail: [sales@venuswww.demon.co.uk](mailto:sales@venuswww.demon.co.uk)



CQ...CQ! Call in on the

## GOOD NEWS

### CHRISTIAN NETS

Every Sunday at 8am and 2pm on 3747 kHz or 144.205 MHz at 3pm, sharing Christian fellowship over the air.



For more information telephone 01803 854504 or write to our Membership Secretary

## WACRAL

51 Alma Road, Brixham, South Devon, TQ5 8QR See Internet Web Page [HTTP://www.G0PPQ.demon.co.uk](http://www.G0PPQ.demon.co.uk)

## MS-WINDOWS HF PROPAGATION SOFTWARE

ASAPS Professional Grade HF Propagation prediction software from IPS Radio and Space Services. Uses IPS and CCIR ionospheric models for the ultimate in HF prediction - Used by the professionals! GRAFEX table/graph, frequency plan, field strength predictions, batch file operation, on-line user's guide. Requires at least 386 PC with MS-Windows 3.1 or higher, 8MB of disk space, SVGA display. Only £170 plus £2.50 P&P (UK) or £5 P&P elsewhere.

For full details send a large SAE to Simon Collings, Radio Communications Consultant, 46 St Michaels Road, Cheltenham, Gloucestershire GL51 5RR. Tel/Fax: 01242 514429. E-mail: [scollin@sapphire.win-uk.net](mailto:scollin@sapphire.win-uk.net) Website: <http://www.sapphire.win-uk.net/> Visa, Access, Mastercard, Eurocard, Delta credit cards accepted.

## HANDS KITS FOR RF CONSTRUCTORS

★ ★ ★ NEW KIT ★ ★ ★

DD.S2 Synthesised VFO 5-6, 6-5 + Sig Gen 0-15 MHz 2 x 16 LCD display with RIT, MODE & BAND. Accuracy to 1 Hz master clock. Full kit £110.

WE HAVE LOTS OF KITS FOR HOMEBREWERS: Tx's, Rx's, DISPLAYS ETC

## HANDS ELECTRONICS

TEGRYN, LLANFYRNACH, DYFED, SA35 0BL. TEL: 01239 698427

FREE CATALOGUE send 2 x 2nd class stamps

## Clear English for high-technology companies

- ☐ Clear user manuals ☐ Readable reports
- ☐ Effective sales literature

## IFW Technical Services

G3SEK

01235 535981

<http://www.ifwtech.demon.co.uk>

## DELTA COMMUNICATOR


Professional range of amateur antennas for 10-15-20m. 3 element £265, 2 element £205, rotary dipole £98

Quality built antennas direct from the manufacturer - save POUNDS!

Telephone 01269 843639 for details

# The Phasing Transceiver on 73kHz

*The concluding part by John R Hey, G3TDZ\**

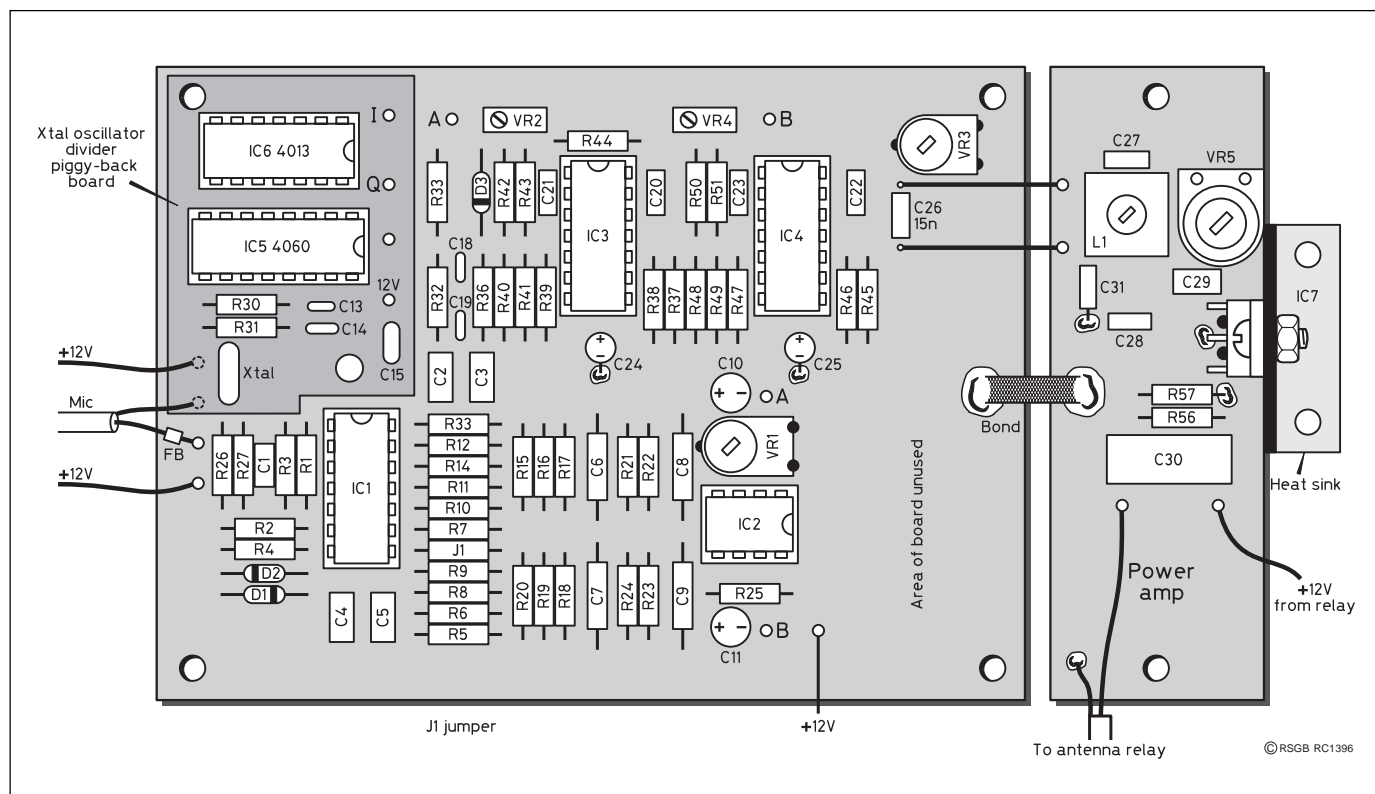

**Fig 3: Transmitter board showing the component layout with the crystal oscillator divider piggy-back board in the top left-hand corner.**

**P**ORTABLE OPERATION seemed to require attention and to this end, battery power was decided on; a 12V jelly battery worked well. Because of this, the regulators in the receiver and VFO were lowered to 9V. Without these, chaos breaks loose.

As sideband switching now takes place at the oscillator drive, in the receiver, the original sideband switch is not needed; the USB pin should be connected to the sideband switch pin by a hidden wire under the board.

On the exciter where the VFO amplifier and RF phasing network used to be, there is just room for the divider piggy-back board to be mounted, see **Fig 3**. The output transformer and converter are not fitted and their space left blank. As mentioned in part one, the tuned circuit is now fitted on the power amp board. Here a small piece of thick aluminium bolted to the chassis forms a heat sink for the PA stage TDA2003.

A four-pole relay energised from the PTT changes over the antenna, earths the receiver

on transmit, mutes the receiver audio on transmit, and powers up the PA. An LED indicates the transmit condition.

A mechanical dial with a 5:1 or even 3:1 slow drive is adequate. Coverage is from 71kHz to 75kHz with about 500Hz overscan.

Use of an op-amp for an RF stage where gain can so easily be specified enables a pot in the feedback return to adjust RF gain.

## SETTING UP

IF A COUNTER is available, adjust the VFO coil core (**Fig 4**) so that at tuner mid travel, a reading of 73kHz results at either I or Q terminals or at pin 4 of the 4060. Place a 'scope probe on pin 12 of IC1 and adjust RV1 for minimum signal. Similarly with probe on pin 12 of IC2, adjust RV2 for minimum signal.

Into the antenna socket inject a 73kHz low level signal and tune in to hear a note. Use the lowest level consistent with a clear tone. Tune L1 for maximum. Selecting the other sideband, the tone should all but vanish, but will reappear the other side of zero beat. Advance the RF

gain and back off the input. Somewhere just before maximum gain the point of best S/N ratio is achieved. Peak L1 for maximum.

Slowly increase the injection to a point where further increase does not produce a corresponding increase in audio. Adjust the S meter pot for a reading of S9. This completes the receiver alignment.

Transmitter alignment is no more difficult. Connect a 'scope probe to the top of RV5. Adjust L1 for maximum signal. Adjust RV2 for minimum signal; do the same for RV4. Repeat these last two operations, raising 'scope sensitivity till just a line remains. If a two tone generator is not to hand, a single tone audio generator should be fed into the mic input. A sine wave at 73kHz should result at RV5 top, if at this stage a bit raggy. Adjust both RV3 and RV1 till the sine wave becomes clean. With a two-tone generator, these operations are adjusted for the purest waveform.

Connect an antenna and microphone. Connect the 'scope, with Y amp set to its least sensitive, to the junction of L and C on the antenna loop. Speaking into the mic at normal

\*8 Armley Grange Crescent, Leeds LS12 3QL



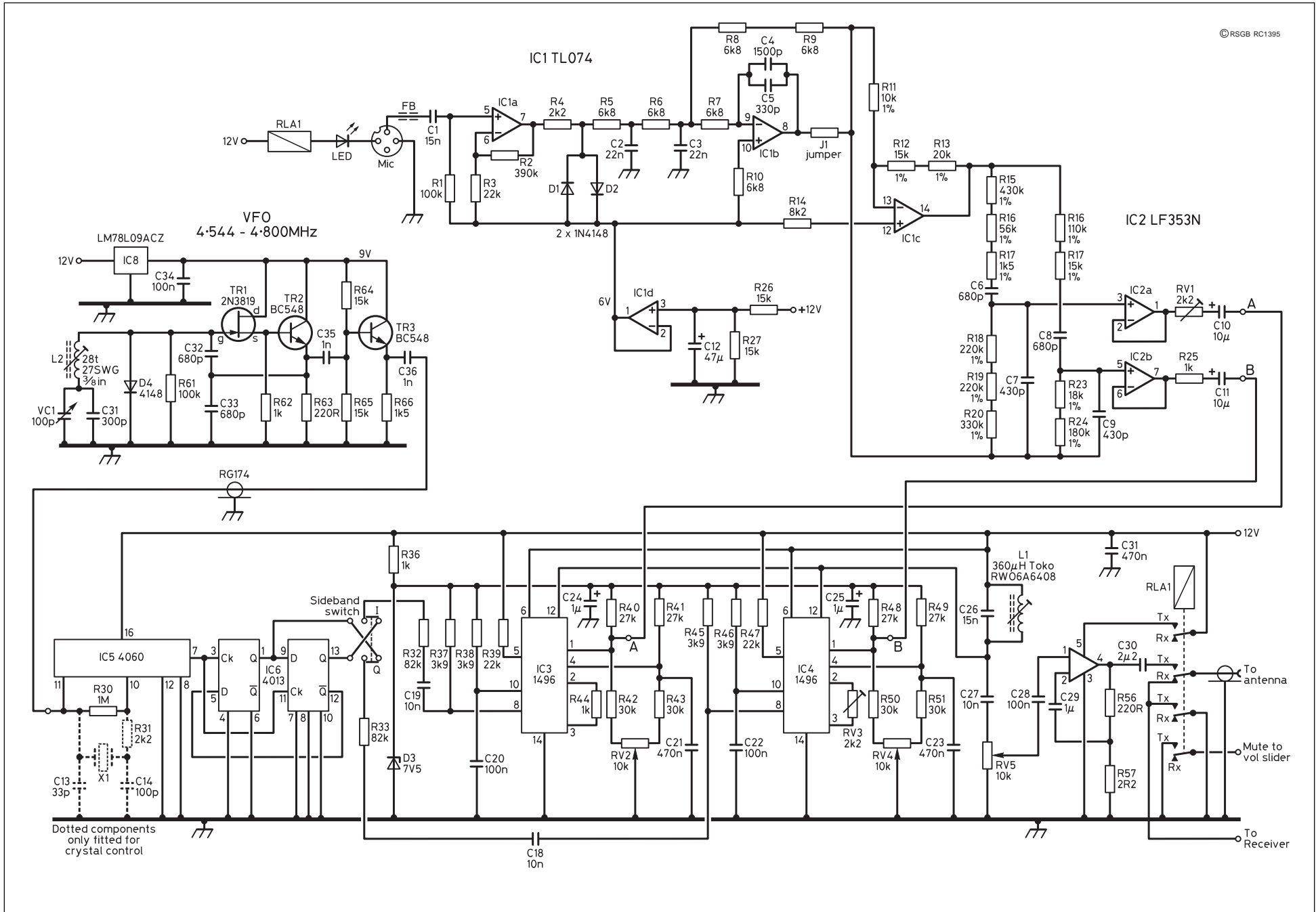


Fig 4: Circuit diagram of the transmitter.

## AERIAL ROTOR FOR ONLY £49.95!



**AR300XL Aerial Rotor, Control Unit and Optional Alignment Bearing**

Rotor unit type AR300XL and control console. Continuous indication of beam heading. Clamps to 2in (52mm) max. mast and takes 1 1/2in (38mm) max. stub mast. 'Offset' type mounting. Vertical load carrying 45kg. Special offer £49.95 plus £4.95 p&p.

**AR1201 Alignment (support) bearing.** Allows greater/higher head loads. Fitted above rotor £18.95.

RR-50 Manually tuned satellite receiver. ideal ATV 1.3GHz use and DIXING 1F coverage 950-1750MHz, video bandwidth 12-26MHz adjustable £199 DELUXE Model with Threshold Assistance board fitted (threshold 3.5dB) £329

### CATALOGUE

Send £1 for our latest glossy 34 page catalogue, which you will receive back by return of post.



## AERIAL TECHNIQUES

11 Kent Road, Parkstone, Poole, Dorset BH12 2EH.

Tel: 01202 738232 Fax: 01202 716951

## J. BIRKETT

25 The Strait, Lincoln LN2 1JF

Tel: (01522) 520767

(Partners: J. H. Birkett, J. L. Birkett)

Suppliers of Electronic Components

RACAL H.F. TRANSMITTER-RECEIVER 3 to 30 MHz USB PA 20 Watt, Input 240V A.C. or 24 Volt D.C. Contains 3 Units Tx-Rx, Decoder-Decoder, PA-Power Pack, Tx-Rx Tuner by Thumbwheel switches. No Leads. Not much info. Operators Handbook. Interesting. @ £125 (P&P £20).

R.F. POWER TRANSISTORS SD1487 100 Watt SSB, 12 Volt with Data @ £12.95 (£22 Pair), SD1285 @ £7.00, SD1480 @ £8.50.

AIR SPACED VARIABLE CAPACITORS 330-360pF 3/16" Spindle @ £2.50, 5 for £10.00

SILVER PLATED CERAMIC ROTARY SWITCHES 3 Pole 3 Way @ £2.50.

FERRITE RODS 6"x3/8" @ £1.50, 6"x1/2" with coils @ £3.3"x1/2" with coils @ 50p.

UHF POWER AMPLIFIER 900MHz with Mitsubishi Module M67701 @ £5 (P&P £2.50).

C804 TYPE VARIABLE CAPACITORS 10pF, 25pF, 50pF, 100pF. All at £3.50 each.

SURPLUS DIE CAST BOXES Approx. size 3x1 1/2" @ £1, 4x3 1/2" @ £1.95, 7x4 1/2" @ £4.50, 7x4 1/2" @ £4.75.

MOST USEFUL AIR SPACED VARIABLE CAPACITOR 200-300pF. Can be used as Single 500pF or 200pF or 300pF @ £3.50.

EX-AIRFORCE VHF TRANSMITTER 1985 10 Channel No Control Box, 21 Valves, Dynamometer etc. @ £30 (P&P £8.50).

DISC CERAMICS 3.9, 4.7, 5.6, 9.1, 12, 15, 22, 27, 33, 47, 51, 82, 120pF 1Kw. All at 15p each, 2500pF 7.5Kw @ 50p, 0.01uF 7.5Kw @ £1.

ELECTRICAL PARAMETRIC ALTIMETER MK22D @ £16 (P&P £6), AIR SPEED INDICATOR 450 Knots @ £10.

Access, Switch, Barclay Card and American Express cards accepted, P&P £1 under £10, Over Free, Unless otherwise stated.

C.M. HOWES KITS Available by post and for callers.

## Essex Amateur Radio Services

The little dealer with the big heart

### BUYERS ARE WAITING NOW FOR YOUR PRE-ENJOYED EQUIPMENT!

\* VHF/UHF \*

\* HF Transceivers \*

\* Station Accessories \*

### AVOID Part Exchange WE PAY TOP PRICES

We pay cash same day or 24 hours by post.

Always large stock available. Phone today for the best deals.

Silent Key sales handled efficiently and personally.

4 Northern Avenue, Benfleet

Essex SS7 5SN

Telephone

**01268 752522**

7 days a week 8am to 8pm

## WISE BUY



## BARGAINS!

ALL PRICES INCLUDE P&P + VAT

PYE M294e, 'E' band, 3 ch crystal controlled, ideal 4m packet, etc., supplied with MIC + L/S.....£30

PYE M294, 'A' - high band 1 ch crystal controlled, ideal 2m packet, etc., supplied with MIC + L/S.....£35

STORNO 5662S UHF synthesised 12v mobiles, supplied with pre-programmed Epm, BCD switches and full info to make 100ch, 15w, mobile for 70cms, just needs 2 crystals. MIC L/S to complete.....£45

SMC 317L6 high band fm, h/holds, similar to Yaesu FT202, 6 ch, crystal controlled for 2m with desktop charger, N1-CAD.....£30

UHF 1/4 wave whips for h/holds with BNC plug - new and uncut, will tune approx 410MHz upwards.....2 for £12

PYE P5000 series single desktop chargers, unused, boxed.....£20

AIRLITE 62 head/mic sets, supplied in used/serviceable condition.....£15

AIRLITE 62 as above but as new/boxed last few.....£30

1 ONLY - Marconi Appollo solid state marine receiver.....£300

All goods are supplied in "as is" condition but are checked for completeness before despatch.

All prices include UK mainland p/p - Access/Visa orders welcome

Technical Modification enquiries after 4.30p.m. please or see.

## G.W.M. RADIO LTD

40/42 PORTLAND ROAD, WORTHING, SUSSEX BN11 1QN

TELEPHONE: 01903 234897 FAX: 01903 239050



## HATELY ANTENNA TECHNOLOGY

## GM3HAT

1 Kenfield Place, ABERDEEN AB15 7UW Tel & Fax: 01224 316 004

### CROSSED FIELD ANTENNAS MORE HEALTHY

Thanks to our policy of continuous research we are happy to announce that an apparently trivial and yet subtle change to the termination components within our DELAY LINE RADIATORS and our CROSSED FIELD LOOPS has resulted in a marked improvement to performance.

The changes are actually a slight simplification so can be incorporated at the same prices. In fact the Crossed Field Loop is physically slimmer to a single metal loop which is to be supported horizontally, and gives all round radiation on all HF Bands.

For those hesitating to send an order, we can assure you that the time is arrived in which to place an order. As we will be spending the time between the typing of this order and the publication date, in supplying free retro-fit units to earlier purchasers, be positive and telephone us your order without delay. Remember no mast needed; just a house to slide underneath the antenna and as a place for the shack and a mains connection!

EMDR 1 for bungalows £218 EMDR 2 for 2 or 3 storey homes £230  
CFL 1 for flats £250

## PC KITS and PC BITS


From a 486SX Barebone up to a 200MHz Pentium Pro system our PC Kits and Barebones (case, power supply and motherboard) come with step by step assembly instructions and we are happy to tailor the configuration to meet a specific upgrade requirement, to fit in with parts you may have or would prefer to buy from someone else.

**A FEW of OUR BITS:-** Motherboards - 33 different motherboards (ISA, EISA, VL bus and PCI) from 386SX to 200MHz Pentium Pro. Cases - 14 different cases in our range from £50 including series of fully R.F. suppressed cases and PSUs up to 10 bay tower with 300W PSU Power Supplies - 15 different power supplies to fit most types of cases, from £35. If we can't supply one we can normally repair your's Display Adaptors - MGA/CGA/EGA and 16 different VGA cards for all bus types, from 256K ISA VGA up to 8Mb PCI inc range of economical cards. Controllers and I/O - 30 different types of controllers and I/O card for all types of bus (8-bit, 16-bit, VL, EISA, PCI) for just about every sort of device and most I/O requirements inc special serial cards to use IRQ 10-15, high speed serial and parallel ports.....and many, many other items.

Prices Exclude VAT and Delivery. Credit Cards and Public Sector P.O.s accepted (credit cards not charged till dispatch of goods), orders subject to 3TH Ltd conditions of sale

So if you are thinking about building or enhancing your own machine, then for a brochure, price lists, spec lists etc. contact:-

**3TH Ltd, 48 Hutchcomb Rd Oxford OX2 9HL Tel 01865 791452 Fax 01865 794267**

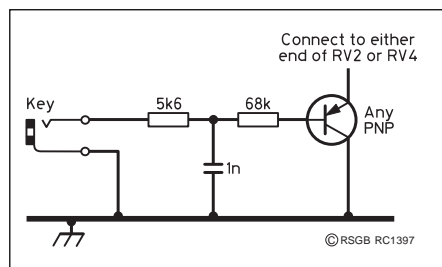

**Fig 5: The 73kHz phasing transceiver can operate on CW using this keying method.**

level, increase RV5 till the typical SSB waveform is seen to just begin flat topping. The very high Q of the antenna will produce voltages in excess of 240V AC and clean up any roughness in the waveform. An unloaded Q of 81 was measured on the prototype antenna and when connected to the transmitter, a Q of 60 was found. This should reduce the audio bandwidth, but in practice it sounds very good indeed.

## OPERATION

MOST OPERATORS WILL be looking towards CW on this band. A simple keying method is to unbalance one of the modulators by turning on a PNP transistor with key down (Fig 5). It is usually easier to send good Morse if you can hear the tone. A better method therefore might be to construct a Morse oscillator and feed this into the microphone socket.

## SSB AND CAVING

THE CIRCUIT DESCRIBED has been used as a cave radio [see page 56 - Ed]. Crystal control is used in place of the VFO, the S meter circuit may be omitted, and the CW filter disabled by omitting C36 and C37. The CW/SSB switch is permanently wired to SSB under the board. A crystal must be chosen to coincide with one band edge, having chosen your sideband.

The cave radio was constructed in 18 gauge tin plated steel where chassis members were bolted and sweated together. With a waterproof steel case, a mylar speaker, rubber dollies fitted to the switches and the sockets sealed, a reasonably cave-proof set resulted, but just for extra strength was carried in an ammunition case. A chassis drawing is available from the author.

The antenna loop used for underground has Terry clips to hold the wires to the wooden supports for easy dismantling and reassembly. With a multi-turn loop, at the expense of the E wave, the magnetic field is enhanced. One may consider the two loops as primary and secondary of a transformer separated by a few hundred feet of limestone. The signal strength falls off according to an inverse cube law, that is it loses 18dB every time the distance is doubled. A maximum range of 650ft is in theory possible, but about 400ft can be relied upon.

For the amateur looking for DX, the small PA can drive a much larger beast. For ultra slow narrow band Morse or data modes, it is possible to insert a sharp filter at the CW/SSB switch terminals. Much is yet to be written on these finer methods. Meanwhile, the phasing rig makes an easy to get going box of tricks with a proven track record speleologically. ♦

## COMPONENTS

### Parts list for Modified Receiver Section (Fig 2)

Resistors:	
R1	10k
R2	270
R3	5k6
R4, 11, 31, 39	1k
R5, 12, 28, 30, 36, 38	470
R6, R7, 13, 14, 32, 33, 40, 41	2k2
R8, 15	22k
R9, 10, 16, 17	30k
R26, 27, 34, 35	3k9
R29, 37	560
RV1, RV2	10k 3/8 in Multiturn trimpot
RV3 (Piggy-back board)	1k trimpot or front mounting control (long spindle)

Capacitors:	
C1	15n polyester
C2	220n polyester
C3, C8, C9	1n ceramic plate
C4	470n monolithic (multilayer)
C10, 11, 16, 17	100n monolithic (multilayer)
C18, 19	22n polyester
C51, 52	1µ Tant.

Semiconductors:	
IC1, IC2	MC1496

**Other items:**  
See original article for full receiver component list.

### Parts list for Transmitter Section (Fig 4)

Resistors:	
R1, R61	100k
R2	390k
R3, 39, 47	22k
R4, 31	2k2
R5, 6, 7, 8, 9, 10	6k8
R11	10k
R12, 22	15k
R13	20k
R14	8k2
R15	430k
R16	56k
R17	1k5
R18, 19	220k
R20	330k
R21	110k
R23	18k
R24	180k
R25, 36, 44, 62	1k
R26, 27, 64, 65	15k
R30	1M

Resistors:	
R32, 33	82k
R37, 38, 45, 46	3k9
R40, 41, 48, 49	27k
R42, 43, 50, 51	30k
R56, 63	220
R57	2R2
R66	1k5
RV1, RV3	2k2 cermet horiz. trimpot
RV2, RV4	10k 3/8 in multiturn trimpot
R5	10k cermet horiz. trimpot

Capacitors:	
C1, 26	15n polyester
C2, C3	22n polyester
C4	1500p polypropylene (green Wima)
C5	330p polypropylene (green Wima)
C6, C8, 32, 33	680p polystyrene
C7, C9	430p polystyrene
C10, 11	10µ 16V tant.
C12	47µ 16V radial electrolytic only fitted for crystal control.
C13 and C14	100n monolithic (multilayer)
C15, 20, 22	10n ceramic disc
C18, 19	470n monolithic
C21, 23	1µ tant
C24, 25	10n polyester
C27	100n polyester
C28, 34	1µ polyester
C29	2µ2 400V polyester
C30	300p polystyrene
C31	1n ceramic plate
C35, 36	

Semiconductors:	
IC1	TL074
IC2	LF353N, AD712, 4558 etc.
IC3, IC4	MC1496
IC5	CD4060BCN
IC6	CD4013BCN
IC7	TDA2003V
IC8	LM78L09ACZ
Tr1	2N3819
Tr2, Tr3	BZX79C7V5

Other items:	
L1	Toko RW06A6408 (Cirkit, Bonex)
L2	3/8" Aladdin former 28t, 27SWG
VC1	100p tuner (found at rallies)
RLY1	12V 4 pole changeover 2A
Ant Socket	SO259
Battery	12V 1.2AH Jelly rechargeable.
Sideband Switch	2 pole changeover miniature toggle
Case	Maplin XJ34M

## 73kHz NEWS

### LF Record Increased Again

THE ONE-WAY 73kHz distance record has been dramatically extended from around 22km to 100km. On 12 April, Julian Gannaway, G3YGF/P, located near Rampisham in Dorset, received a 73kHz CW signal from Andy Talbot, G4JNT, near Southampton. Julian received an RST 319 signal from Andy, who was using 100W input to a 6m high 'T' antenna.

It is suggested that all those who can transmit on 73kHz should do so at

11.00am and / or 11.00pm for about 15 minutes any day of the week, but especially Saturday and Sunday. To help experimenters, listeners are urged to send reception reports on all 73kHz-band signals heard by the quickest means possible.

### LF in SF

TIMO KIINSI, OH1TH, tells us that from 1 April, Finnish amateurs may use 135.7 - 137.8kHz with 100W power. It was not clear if this was on a special permit basis, or if there were other restrictions.